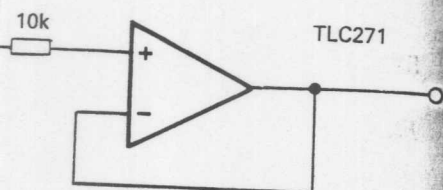



sample and hold.



$$\text{Drift rate } \frac{dV}{dt} = \frac{I_{LEAK}}{C}$$


See Ref. 1

sample and hold.

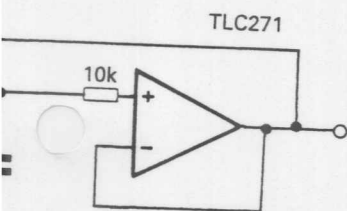


See Ref. 1

y sample and hold.

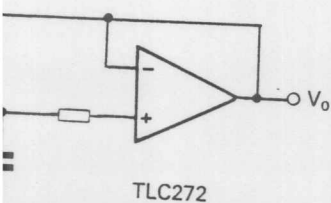

See Ref. 1

Fig. 5.6 Fast sample and hold.

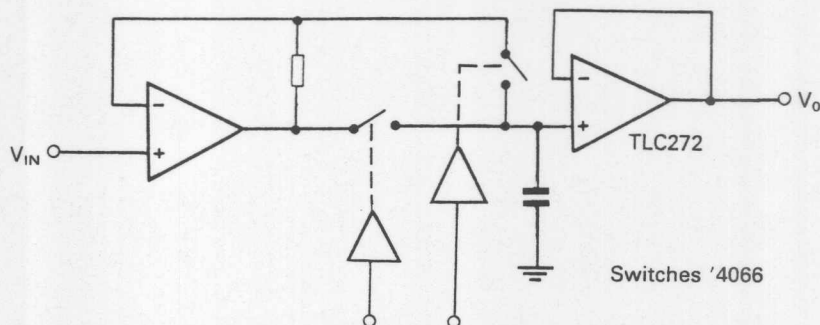

RECTIFIERS

Fig. 5.7 Precision full wave rectifier (absolute value circuit).

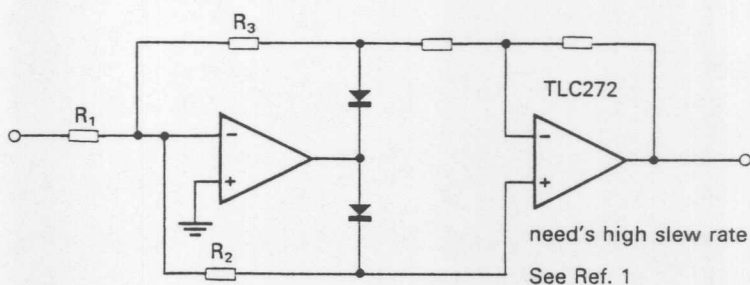


Fig. 5.8 Halfwave rectifier.

